

# Circuit Documentation

## Summary of the Circuit

This circuit is designed to control a red LED using an Arduino UNO. The LED is connected to the Arduino through a 220 Ohm resistor. The Arduino is programmed to blink the LED on and off at one-second intervals.

## Component List

1. **LED: Two Pin (red)**
  - **Description:** A standard red LED with two pins: anode and cathode.
  - **Purpose:** To emit light when powered.
2. **Arduino UNO**
  - **Description:** A microcontroller board based on the ATmega328P.
  - **Purpose:** To control the LED by providing the necessary logic and power.
3. **Resistor**
  - **Description:** A 220 Ohm resistor.
  - **Purpose:** To limit the current flowing through the LED, preventing it from burning out.

## Wiring Details

### LED: Two Pin (red)

- **Cathode:** Connected to the Resistor's pin2.
- **Anode:** Connected to the Arduino UNO's GND pin.

---

### Arduino UNO

- **GND:** Connected to the LED's anode.
- **D13:** Connected to the Resistor's pin1.

---

### Resistor

- **Pin1:** Connected to the Arduino UNO's D13 pin.
  - **Pin2:** Connected to the LED's cathode.
- 

## Documented Code

The following code is uploaded to the Arduino UNO to control the LED:

```


void setup() {
  pinMode(LED_BUILTIN, OUTPUT);
}
void loop() {
  digitalWrite(LED_BUILTIN, HIGH);
  delay(1000);
  digitalWrite(LED_BUILTIN, LOW);
  delay(1000);
}

```

## Code Explanation

- **setup() Function:** This function runs once when the program starts. It sets the built-in LED pin (D13) as an output.
- **loop() Function:** This function runs continuously after setup(). It turns the LED on for one second, then off for one second, creating a blinking effect.

This code utilizes the built-in LED pin (D13) on the Arduino UNO to control the external LED connected to the same pin. The delay(1000) function is used to create a one-second interval between turning the LED on and off.

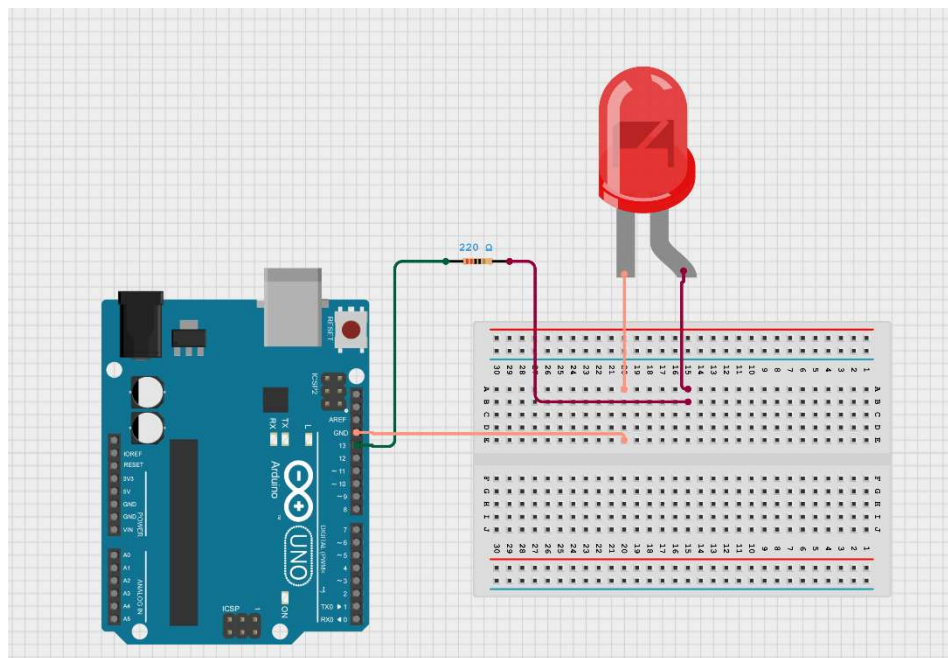

*Fig 1*